 


1. (a) Using the minimum 2-level SoP logic required, design a sequential circuit with three T flip-flops, A, B and C, and two inputs E and X that performs as follows:
 - If $E = 0$ the circuit remains in the same state regardless the value of X,
 - When $E = 1$ and $X = 1$ the circuit goes through the state transitions 000 to 001 to 010 to 011 to 100 back to 000, and repeats,
 - When $E = 1$ and $X = 0$ the circuit goes through the state transitions 111 to 110 to 101 to 100 to 011 back to 111, and repeats.


- (b) Is the countup self-starting, *i.e.* if X remains at 1? Justify. Include state transition diagram.
- (c) Is the countdown self-starting, *i.e.* if X remains at 0? Justify. Include state transition diagram.

2. The finite state machine (FSM) shown in the figure below is implemented with one toggle (T) flip-flop and one JK flip-flop. It has one input I and one output Z. The combinational logic required for the next state and output functions is implemented by a PLA structure.

- (a) Write the logic expressions for J_A , K_A , T_B and Z.
- (b) Which of the two types of FSM seen in classes is this? Justify.
- (c) Obtain the state transition table including the output Z.
- (d) Draw the complete state transition diagram of the FSM.



 - (e) Assuming the \overline{PR} is deasserted (HIGH) and the active-low clear \overline{CLR} below is connected to both flip-flops fill the timing diagram below for Q_A , Q_B & Z.



3. Design a Mealy finite state machine with input X and output Z. The output Z should be asserted for one clock cycle whenever the sequence ...0111 or ...1000 has been input on X. The patterns may overlap. For example, X = ...0000111000...should generate the output stream Y = ...0000001001...

- Complete the state diagram for the sequence detector, without concern for state minimization;
- Minimize the number of states;
- Use the state assignment guidelines to obtain a good state assignment for the reduced state machine.
- Implement your encoded, reduced state table and show all the minimized logic equations for the next state and outputs.
- Implement this Mealy finite state machine with DFFs.