

DALHOUSIE UNIVERSITY
Department of Electrical & Computer Engineering
ECED 2200 - Digital Circuits

Final Examination

Winter 2013

Name: _____

Student ID: _____

Marks: Total marks out of 50

Question	Marks
1	10
2	10
3	10
4	10
5	10
Total	50

1.- Two Boolean functions are given below, f_1 is given using the shorthand minterm form and f_2 is given using the shorthand maxterm form.

$$(i) f_1(A, B, C, D) = \sum m_i(0,1,2,3,8,10,12,14)$$


$$(ii) f_2(A, B, C, D) = \prod M_i(6,7,8,12,13,15)$$

- (a) Use K-maps to find the simplest sum-of-products (SoP) expression for f_1 and the simplest product-of-sums (PoS) expression for f_2 . [6 pts]
- (b) Find hazard-free implementations for f_1 in SoP and f_2 in PoS. [4 pts]

- 2.- (a) Draw the circuit for a 4-bit shift register using D flip-flops that can perform parallel-to-serial conversion as well as serial-to-parallel conversion. [6 pts]
- (b) In your diagram, identify:
- i) The serial input terminal,
 - ii) The serial output terminal,
 - iii) The parallel input terminals, and
 - iv) The parallel output terminals. [4 pts]
- 3.- (a) Provide the state transition table for an asynchronous binary up-counter that goes through the sequence 0000, 0001, 0010, ..., 1110, 1111, 0000, 0001, [2 pts]
- (b) Draw the ripple binary up-counter in (a) using T flip-flops. [3 pts]
- (c) Provide the state transition table for a decade up-counter. [2 pts]
- (d) Build the asynchronous decade binary up-counter in (c) using T flip-flops. [3 pts]
- Hint: Modify the counter in (b) such that it turns into a decade counter.*
- 4.- Use JK flip-flops to design a finite state machine (FSM) that works as a 2-bit binary synchronous up-counter when its input $X = 0$ and as a 2-bit binary synchronous down-counter when its input $X = 1$.
- (a) Draw the state transition diagram. [2 pts]
 - (b) Build the state transition table. Include values of flip-flop inputs. [3 pts]
 - (c) Find minimized logic expressions for flip-flop inputs. [3 pts]
 - (d) Draw the resulting logic circuit that implements this FSM. [2 pts]
- Note: Please find flip-flop excitation tables attached in the last page.*

5.- The following circuit contains two RS flip-flops.

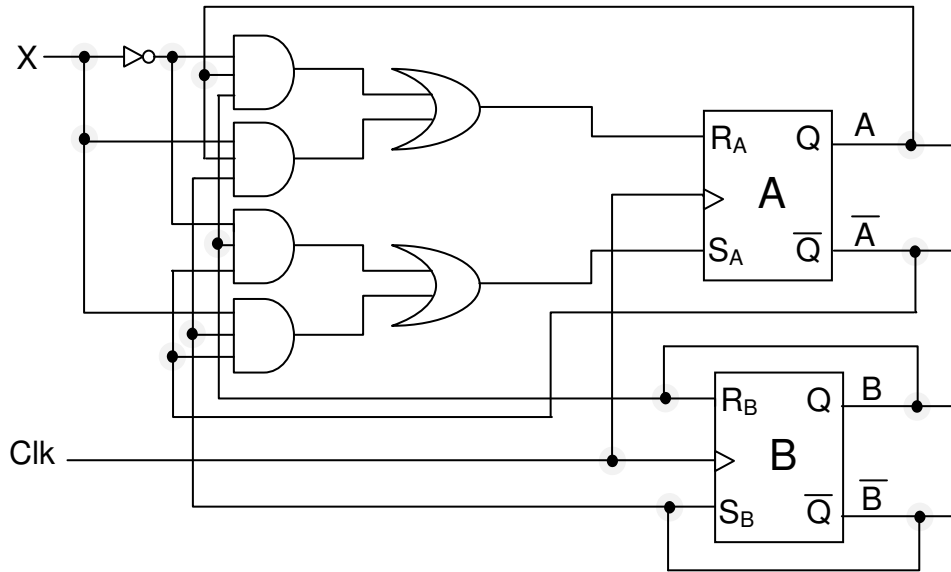- (a) Write the logic expressions for R_A , S_A , R_B and S_B . [2 pts]
- (b) Obtain the state transition table for the circuit. [3 pts]
- (c) Sketch the state transition diagram for the circuit. [2 pts]
- (d) Compare RS and JK flip-flops, relationship and advantage of one type over the other in light of the results obtained for this question and question 4 above. [3 pts]



Excitation Table

Q	Q+	R	S	J	K	T	D
0	0	X	0	0	X	0	0
0	1	0	1	1	X	1	1
1	0	1	0	X	1	1	0
1	1	0	X	X	0	0	1

Basic Boolean Identities

	<u>Identity</u>	<u>Comments</u>
1.	$A + 0 = A$	Operations with 0 and 1
2.	$A + 1 = 1$	Operations with 0 and 1
3.	$A + A = A$	Idempotent
4.	$A + \bar{A} = 1$	Complementarity
5.	$A \cdot 0 = 0$	Operations with 0 and 1
6.	$A \cdot 1 = A$	Operations with 0 and 1
7.	$A \cdot A = A$	Idempotent
8.	$A \cdot \bar{A} = 0$	Complementarity
9.	$\bar{\bar{A}} = A$	Involution
10.	$A + B = B + A$	Commutative
11.	$A \cdot B = B \cdot A$	Commutative
12.	$A + (B + C) = (A + B) + C = A + B + C$	Associative
13.	$A \cdot (B \cdot C) = (A \cdot B) \cdot C = A \cdot B \cdot C$	Associative
14.	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	Distributive
15.	$A + (B \cdot C) = (A + B) \cdot (A + C)$	Distributive
16.	$A + (A \cdot B) = A$	Absorption
17.	$A \cdot (A + B) = A$	Absorption
18.	$(A \cdot B) + (\bar{A} \cdot C) + (B \cdot C) = (A \cdot B) + (\bar{A} \cdot C)$	Consensus
19.	$\overline{A + B + C + \dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \dots$	De Morgan
20.	$\overline{A \cdot B \cdot C \cdot \dots} = \bar{A} + \bar{B} + \bar{C} + \dots$	De Morgan
21.	$(A + \bar{B}) \cdot B = A \cdot B$	Simplification
22.	$(A \cdot \bar{B}) + B = A + B$	Simplification