

DALHOUSIE UNIVERSITY
 Department of Electrical & Computer Engineering
 ECED 2200 - Digital Circuits

Final Examination

Winter 2016/2017

Name: _____

Student ID: _____

Marks: Total marks out of 45

Question	Subject	Worth	Score	Outcome Achievement
1	Multiple-choice questions	10		-----
2	Counters	12		-----
3	Sequential circuit	9		-----
4*	Finite State Machines	14		
Total		45		-----

*Note: Question 4 is designed to evaluate course outcome 04B (i.e. Conceptualize and evaluate alternative approaches; perform appropriate design to fit requirements).

Excitation Table


Q	Q+	R	S	J	K	T	D
0	0	X	0	0	X	0	0
0	1	0	1	1	X	1	1
1	0	1	0	X	1	1	0
1	1	0	X	X	0	0	1

Q1. Multiple-choice questions. Circle **ONLY ONE** that apply. [1 pt each]

(1) How can the cross-coupled NAND RS latch used in Lab4 be made to have active-HIGH inputs?

- (a) It can't be done (b) Invert the S-R inputs (c) Invert the Q (d) Invert the clock

 (2) Four (4) D flip-flops are connected in tandem as a Frequency Divider. For a 2 MHz square wave input frequency, determine the frequency of the output:



- (a) 1MHz (b) 500 kHz (c) 125 kHz (d) None of the above

(3) To implement a T flip-flop using a JK flip-flop:

- (a) J=K=1 (b) J=T, K=0 (c) J=T, K=T' (d) J=K=T

(4) A simple memory component can be implemented from:

- (a) cross-coupled ANDs (b) cross-coupled NORs (c) cross-coupled XORs (d) cross-coupled ORs


(5) How many address bits (i.e. the total of row-select lines and column-select lines) would be required to address 16 x 16 RAM cells?

- (a) 4 (b) 8 (c) 16 (d) 256

(6) The bit sequence 0010 is serially entered (right-most bit first) into a 4-bit parallel out shift register that is initially clear. What are the Q outputs after two clock pulses?

- (a) 1000 (b) 0010 (c) 0000 (d) 0001

 (7) For a 4-bit ring counter as shown below, one of the FFs is preset with a 1 and all others are cleared to 0s. How many states does this ring counter have?



- (a) 4 (b) 8 (c) 15 (d) 16

(8) If we add an inverter to the feedback path of the above ring counter, we have a Johnson counter. On the fifth clock pulse, a 4-bit Johnson counter sequence is $Q_3=0, Q_2=1, Q_1=1, Q_0=1$. On the sixth clock pulse, the $Q_3Q_2Q_1Q_0$ sequence is _____.

- (a) 1011 (b) 1000 (c) 0011 (d) 0001


(9) How many flip-flops are necessary to design a state machine with 25 states?

- (a) 4 (b) 5 (c) 25 (d) 2^{25}

(10) Which type of finite state machines has outputs that will only change on the edge of a clock pulse?

- (a) Moore (b) Mealy (c) Mealy-Moore (d) None of the above

 
- Q2. (a)** Design a **synchronous** up counter that goes through the sequence of 000, 001, 010, 011, 100, 101, 000, 001, ... using JK FFs. Show your design steps and draw the final circuit. [4 pts]
(b) Is the counter designed in part (a) self-starting or not? Draw the complete state diagram. [1 pt]
(c) Redesign the counter in part (a) as an **asynchronous** up counter using falling edge triggered JK FFs, **without** using the CLEAR function of the FFs (i.e. modify J, K, and clock for the desired sequence). [4 pts]
(d) The synchronous circuit given below is a pseudo-random counter: [3 pts]




- (d1) Complete the next state equations (i.e. $Q1+$, $Q2+$, $Q3+$), one for each stage (flip-flop).
 (d2) $Q_1Q_2Q_3 = 001$ at initialization. Is the counter self-starting? Draw the state transition diagram.
 (d3) What are the contents of Q_1 , Q_2 , and Q_3 after clocks 20 and 100?

Q3. The FSM shown below has one input I and one output Z . The combinational logic required for the next state and output functions is implemented by a PAL structure.

 - (a) Write the logic expressions for J_A , K_A , T_B and Z . [2 pts]
 (b) Which of the two types of FSM seen in classes is this? Justify. [1 pt]
 (c) Obtain the state transition table including the output Z ; draw the state transition diagram. [3 pts]



 - (d) Assuming an active-low clear \overline{CLR} is connected to both flip-flops, fill the timing diagram below for Q_A , Q_B & Z . [3 pts]



Q4. A pattern detector has one input X and one output Z . The output $Z=1$ whenever either of the sequences “110” or “001” has been detected, overlapping allowed. At all other times Z is set to 0. Note that the machine does not reset once one of the two sequences is detected.

- Implement this pattern detector as a Moore or Mealy FSM; justify your decision. [2 pts]
- Derive the symbolic state table and reduce redundant states. Draw the reduced state transition diagram. [4 pts]
- Use the state assignment guidelines learned in class to obtain a good state assignment for this FSM. [3 pts]
- Implement your encoded FSM using D FFs; show the minimized next-state equations and output Z . [4 pts]
- Draw the pattern detector circuit. [1 pt]