 


ECED 2200 Multiplexers and Flip-Flop Exercise

1. Implement $F(A, B, C) = \sum (1,3,5,6)$ with a 4:1 multiplexer
2. Implement $F(A, B, C, D) = \sum (0, 1,3,4,8,9,15)$ with a 8:1 multiplexer
3. If you only have a 4:1 MUX available, can you implement the function, F, defined by the truth table given below? Draw the MUX and indicate the inputs.

		Q1Q2			
		00	01	11	10
Q3	0	0	1	1	0
	1	1	0	0	1

4. A binary decade up-counter goes through the sequence 0000, 0001, 0010, 0011, 0100, 0101, 0110, 0111, 1000, 1001, 0000, 0001, ...
 - (a) Using the standard design process for synchronous counters, show how to implement this counter using T flip-flops. Include: state transition table and a drawing of the final circuit.
 - (b) Check whether the counter is self-starting or not? Draw the state transition diagram including every possible state.
 - (c) Build an asynchronous (ripple) decade up-counter by modifying a 4-stage ripple binary up-counter using T flip-flops.
 - (d) Sketch the timing diagram of the counter built in (c) for 12 CLK periods. Assume all flip-flops were cleared during the clock cycles preceding time $t=0$. Include:
 - The waveforms CLK_A , CLK_B , CLK_C , & CLK_D , (i.e. the CLK inputs of each flip-flop)
 - The waveforms Q_A , Q_B , Q_C , & Q_D , (i.e. the outputs Q of each each flip-flop)
5. The synchronous circuit given below is a linear feedback shift register (LFSR).



- (a) Complete the next state equations (i.e. $Q1^+$, $Q2^+$, $Q3^+$), one for each stage (flip-flop).
- (b) Assuming that $Q_1Q_2Q_3 = 001$ at $t = 0$ (initialization). Determine the contents of the LFSR after the first, second, third, eighth clock cycles and fill in the table given below.

CLK	Q1	Q2	Q3
	0	0	1

ECED 2200 Multiplexers and Flip-Flop Exercise

1			
2			
3			
4			
5			
6			
7			
8			

- (c) Check whether the counter is self-starting or not? Draw the state transition diagram including every possible state.
- (d) What are the contents of Q1, Q2, and Q3 after clocks 97 and 168?
- 6.** Implement a 4-bit bidirectional shift register with parallel load using DFFs and 4:1 MUXs.