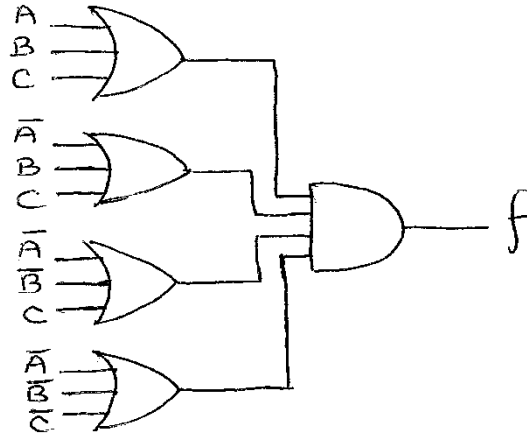


Name: _____

Student ID: _____

Q1.- Consider the function f realized by the logic circuit shown below.

- Analyze the circuit and write the canonical product of sums (PoS) expression for f .
- Use Boolean algebra to simplify the expression of f found in (a) above to its minimized sum of products (SoP) form.
- Use the K-map method to verify the result found in part (b) above.
- Is the minimized SoP expression found hazard-free? Explain and if it is not provide the hazard-free SoP form.



Q2.- Given the following function in sums-of-product (SoP) form:

$$f(A, B, C, D) = \sum m_i(0,1,2,4,5,6,7,8,10)$$

- Prepare its truth table.
- Map the function f in a K-map and identify:
 - One implicant that is not a prime implicant,
 - One prime implicant that is not essential, and
 - All essential prime implicants.

In identifying each implicant above list all the minterms in each of them.

- Write the minimized SoP form for f .

Q3.- Given the multilevel function f below

$$f = \overline{C} \cdot \overline{D} \cdot (\overline{A \cdot B} + B + D)$$

Assume literal complements are available.

- Draw the circuit implementing this function using NOT gates and 2-input AND & OR gates.
- Convert the circuit to NOR-only and draw the circuit for f using only 2-input NOR gates.
- Convert the circuit to NAND-only and draw the circuit for f using only 2-input NAND gates.

Basic Boolean Identities

| | <u>Identity</u> | <u>Comments</u> |
|-----|---|-------------------------|
| 1. | $A + 0 = A$ | Operations with 0 and 1 |
| 2. | $A + 1 = 1$ | Operations with 0 and 1 |
| 3. | $A + A = A$ | Idempotent |
| 4. | $A + \bar{A} = 1$ | Complementarity |
| 5. | $A \cdot 0 = 0$ | Operations with 0 and 1 |
| 6. | $A \cdot 1 = A$ | Operations with 0 and 1 |
| 7. | $A \cdot A = A$ | Idempotent |
| 8. | $A \cdot \bar{A} = 0$ | Complementarity |
| 9. | $\bar{\bar{A}} = A$ | Involution |
| 10. | $A + B = B + A$ | Commutative |
| 11. | $A \cdot B = B \cdot A$ | Commutative |
| 12. | $A + (B + C) = (A + B) + C = A + B + C$ | Associative |
| 13. | $A \cdot (B \cdot C) = (A \cdot B) \cdot C = A \cdot B \cdot C$ | Associative |
| 14. | $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ | Distributive |
| 15. | $A + (B \cdot C) = (A + B) \cdot (A + C)$ | Distributive |
| 16. | $A + (A \cdot B) = A$ | Absorption |
| 17. | $A \cdot (A + B) = A$ | Absorption |
| 18. | $(A \cdot B) + (\bar{A} \cdot C) + (B \cdot C) = (A \cdot B) + (\bar{A} \cdot C)$ | Consensus |
| 19. | $\overline{A + B + C + \dots} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \dots$ | De Morgan |
| 20. | $\overline{\bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \dots} = A + B + C + \dots$ | De Morgan |
| 21. | $(A + \bar{B}) \cdot B = A \cdot B$ | Simplification |
| 22. | $(A \cdot \bar{B}) + B = A + B$ | Simplification |