


1. Synthesize logic circuits to realize the following functions as written (i.e. no logic simplification), use any of the gates seen in classes:

(a) $A \cdot \overline{(A+B)}$,

(b) $\overline{(A+B + A \cdot B)} \cdot \overline{A+B}$

(c) $\overline{(A+B)} \cdot \overline{A \cdot B} \cdot \overline{A \cdot B}$

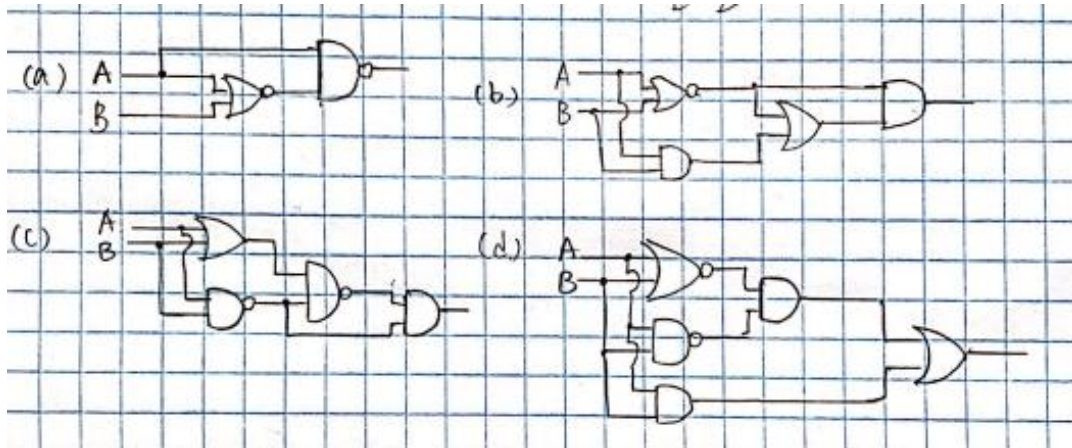(d) $\overline{(A+B)} \cdot \overline{A \cdot B} + A \cdot B$.



2. Use truth tables to prove the following Boolean theorems:

(a) $A \cdot (A+B) = A$,

(b) $A+B \cdot C = (A+B) \cdot (A+C)$.

(c) $A+A \cdot B = A$,

(d) $A+(B+C) = (A+B)+C$.

Example: (a)

A	B	A+B	A(A+B)
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

$A \cdot (A+B) = A$

3. Use Boolean theorems to prove the following identities:

(a) $A \cdot \overline{(A+B)} = A \cdot B$

(b) $A \cdot \overline{B} \cdot C + A \cdot B \cdot C = A \cdot C$

(c) $(A+B) \overline{(A+C)} + B \cdot C = A \cdot C + \overline{A} \cdot B$

(d) $(A+C) \overline{(A+D)} \overline{(B+C)} \overline{(B+D)} = A \cdot B + C \cdot D$

3. (a) $A \cdot (\bar{A} + B) = A \cdot \bar{A} + A \cdot B = A \cdot B$

(b) $A \cdot \bar{B} \cdot C + A \cdot B \cdot C = A \cdot C (\bar{B} + B) = A \cdot C$

(c) $(A+B)(\bar{A}+C) + B \cdot C = A\bar{A} + \bar{A}B + A \cdot C + BC + BC$
 $= A \cdot C + \bar{A} \cdot B + BC = A \cdot C + \bar{A} \cdot B$ (Consensus Identity)

(d) $(A+C)(A+D)(B+C)(B+D) = (A+CD)(B+CD)$ (#15 Distributive)
 $= CD + AB$ (#15 Distributive)

4. Use Boolean algebra to simplify the following expressions:

(a) $\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$

(b) $\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$

4. (a) $\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$
 $= \bar{A}\bar{B}(\bar{C} + C) + A\bar{B}(\bar{C} + C)$
 $= \bar{A}\bar{B} + A\bar{B} = A \oplus B$

(b) $\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D}$
 Rule #3 $= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D$
 $= \bar{A}\bar{B}\bar{C}(\bar{D} + D) + \bar{A}\bar{B}C(\bar{D} + D) + \bar{A}B\bar{C}(\bar{D} + D) + \bar{A}B\bar{C}(\bar{D} + D)$
 $= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}B\bar{C}$
 $= \bar{A}\bar{B}(\bar{C} + C) + \bar{B}\bar{C}(\bar{A} + A)$
 $= \bar{A}\bar{B} + \bar{B}\bar{C}$

	AB	00	01	11	10
CD		1		1	
00					
01		1		1	
11					
10		1		1	

* A Kmap can be used to guide your simplification

5. Consider the functions

$$f_1(A, B, C, D) = \bar{A}BC + (\bar{A} + B + D)(A\bar{B}\bar{D} + B)$$

(a) Find the complements of the functions above and simplify using De Morgan's laws.

$$F = \overline{ABC + (\overline{A+B+D})(AB\overline{D} + B)}$$


$$F = \overline{ABC} \cdot \overline{(\overline{A+B+D})(AB\overline{D} + B)}$$

$$F = (A + \overline{B} + \overline{C}) [\overline{A+B+D} + \overline{AB\overline{D} + B}]$$

$$F = (A + \overline{B} + \overline{C}) (A\overline{B}\overline{D} + \overline{A}\overline{B}\overline{D} \cdot \overline{B})$$


$$F = (A + \overline{B} + \overline{C}) (A\overline{B}\overline{D} + \overline{B} \cdot (\overline{A+B+D}))$$

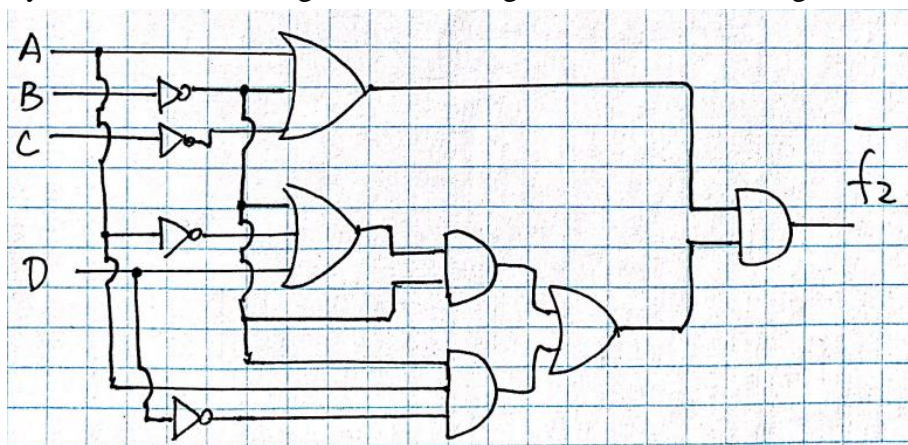(b) Synthesize the resulting functions using AND, OR and NOT gates.



6. (a) Write in binary the following decimals: 6_d , 14.625_d , 27_d , 50.3125_d

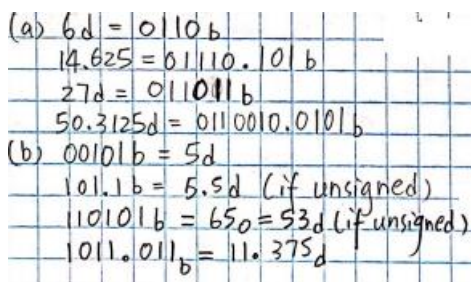(b) Write in decimal the following binaries: 00101_b , 101.1_b , 110101_b , 1011.011_b



7. Express the following decimal numbers using 8-bit signed 2's complement notation:

- i) -25_d , ii) 130_d iii) 17_d , iv) -100_d .

