

VARIABLES by

Q2. Design a counter that goes through the BCD sequence of your **Banner number**. You don't need to include repeated BCD(s). For example, **B00458387** has two repeated numbers '0' and '8'. The required counting sequence is: 0000 (0d) -> 0100 (4d) -> 0101 (5d) -> 1000 (8d) -> 0011 (3d) -> 0111 (7d), then back to 0000 (0d). The underlined numbers are skipped in the counting sequence.

- (a) Using the standard design process for **synchronous** counters, show how to implement this counter using D flip-flops. Please include: state transition table, K-maps, next_state equations, and a drawing of the final circuit. Assuming literal complements are available. [6 pts]
- (b) Is your counter designed in part (a) self-starting or not? Draw the state transition diagram including every possible state. [3 pts]
- (c) Implement one DFF used in part (a) with Master-Slave RS latches. [3 pts]
- (d) Implement one RS latch used in part (c) with logic gates. Please include asynchronous "Preset" and "Clear" for the RS latch. Assume multiple-input logic gates allowed. [3 pts]

(a) D C B A				D ⁺	C ⁺	B ⁺	A ⁺	DC				
								BA	00	01	11	10
0	0	0	0	0	1	0	0	00	0	0	φ	1
0	0	0	1	φ	φ	φ	φ	01	φ	0	φ	φ
0	0	1	0	φ	φ	φ	φ	11	1	0	φ	φ
0	0	1	1	0	1	1	1	10	φ	φ	φ	φ
0	1	0	0	0	1	0	1					
0	1	0	1	1	0	0	0					
0	1	1	0	φ	φ	φ	φ					
0	1	1	1	0	0	0	0					
φ	φ	φ	φ	φ	φ	φ	φ					
OTHERS				φ	φ	φ	φ					


DC				
BA	00	01	11	10
00	0	0	φ	0
01	φ	1	φ	φ
11	0	0	φ	φ
10	φ	φ	φ	φ

DC				
BA	00	01	11	10
00	0	1	φ	1
01	φ	0	φ	φ
11	φ	φ	φ	φ
10	φ	φ	φ	φ

$D^+ = \bar{B}A$

$C^+ = \bar{D}\bar{C} + \bar{D}\bar{A}$

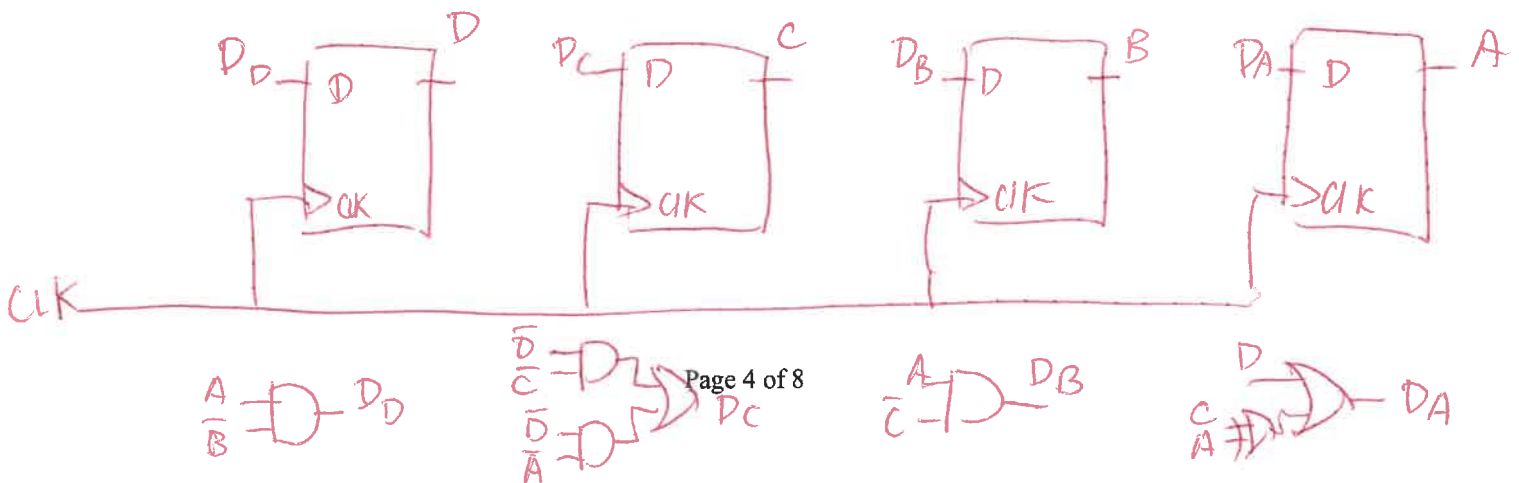$A^+ = D + \bar{C}\bar{A} + \bar{C}A$
 $= D + C \oplus A$



(This page intentionally left blank for your Q2 work)

