
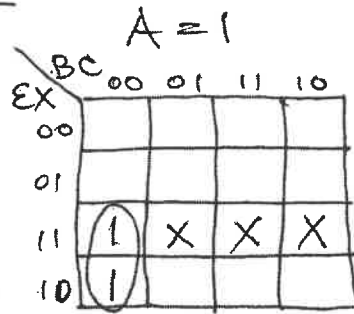




STATE TRANSITION TABLE

Present STATE			INPUTS		NEXT STATE			INPUTS REQUIRED		
A	B	C	E	X	A ⁺	B ⁺	C ⁺	T _A	T _B	T _C
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	0	0
0	0	0	1	0	X	X	X	X	X	X
0	0	0	1	1	0	0	1	0	0	1
0	0	1	0	0	0	0	1	0	0	0
0	0	1	0	1	0	0	1	0	0	0
0	0	1	1	0	X	X	X	X	X	X
0	0	1	1	1	0	1	0	0	1	1
0	1	0	0	0	0	1	0	0	0	0
0	1	0	0	1	0	1	0	0	0	0
0	1	0	1	0	X	X	X	X	X	X
0	1	0	1	1	0	1	1	0	0	1
0	1	1	0	0	0	1	1	0	0	0
0	1	1	0	1	0	1	1	0	0	0
0	1	1	1	0	1	0	0	1	1	1
0	1	1	1	1	1	0	0	1	1	1
1	0	0	0	0	1	0	0	0	0	0
1	0	0	0	1	0	0	0	0	0	0
1	0	0	1	0	0	0	0	1	1	1
1	0	0	1	1	0	0	0	0	0	0
1	0	1	0	0	1	0	1	0	0	0
1	0	1	0	1	X	X	X	X	X	X
1	0	1	1	0	1	1	0	0	0	0
1	0	1	1	1	1	1	0	0	0	0
1	1	0	0	0	1	1	1	0	0	0
1	1	0	0	1	X	X	X	X	X	X
1	1	0	1	0	1	1	1	0	0	0
1	1	0	1	1	X	X	X	X	X	X
1	1	1	0	0	1	1	1	0	0	0
1	1	1	0	1	X	X	X	X	X	X
1	1	1	1	0	1	1	1	0	0	0
1	1	1	1	1	X	X	X	X	X	X

K-map for TA


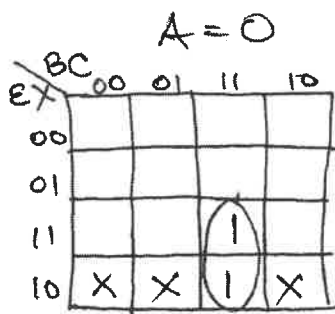

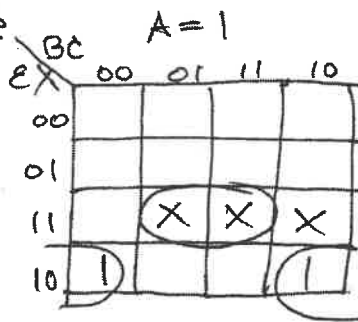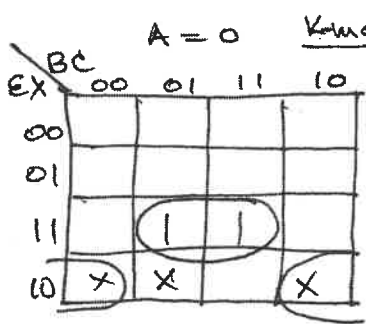
$$TA = \bar{A} \cdot B \cdot C \cdot E + A \cdot \bar{B} \cdot \bar{C} \cdot E$$





$$TB = C \cdot E \cdot X + \bar{C} \cdot E \cdot \bar{X}$$

K-map for TC

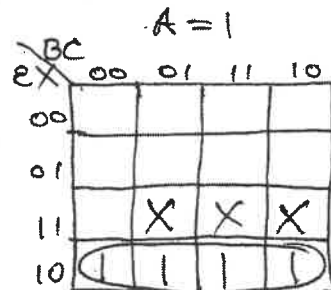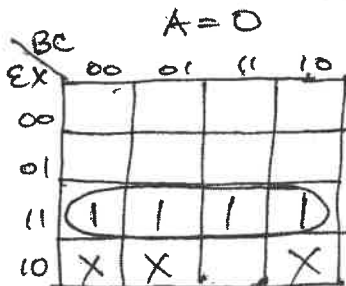
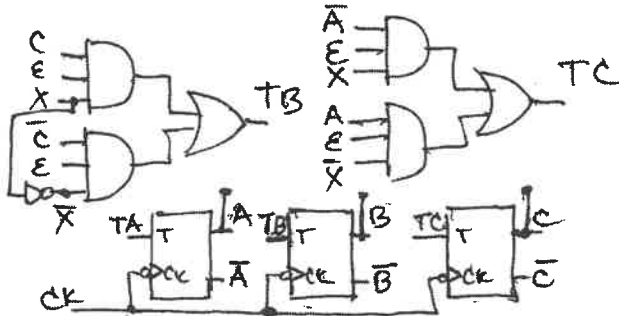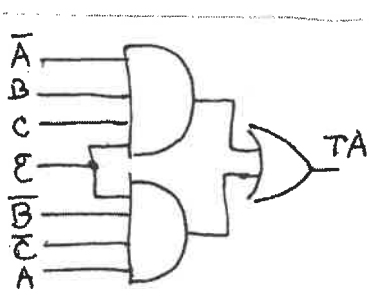
$$TC = \bar{A} \cdot E \cdot X + A \cdot E \cdot \bar{X}$$





(b) & (c)

Assigning 1 to the X's of the implicants used the following is obtained for the unused states:


A	B	C	E	X	TA	TB	TC	A ⁺	B ⁺	C ⁺	
0	0	0	1	0	0	1	0	0	1	0	} Countdown unused states
0	0	1	1	0	0	0	0	0	0	1	
0	1	0	1	0	0	1	0	0	0	0	
1	0	1	1	1	0	1	0	1	1	1	} Countup unused states
1	1	0	1	1	0	0	0	1	1	0	
1	1	1	1	1	0	1	0	1	0	1	

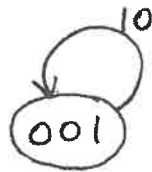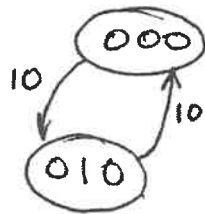For the countdown unused states:
(000, 001, 010)



IT IS NOT SELF-STARTING
Since it never reaches one of the states in the countdown sequence.

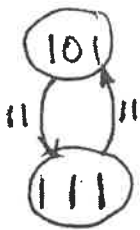For the countup unused states:
(101, 110, 111)



IT IS NOT SELF-STARTING
Since it never reaches one of the states in the countup sequence. It keeps cycling among the unused states.

(a) $K_A = Q_B$

$$\bar{T}_A = Q_B \cdot \bar{I} + \bar{Q}_B \cdot I = Q_B \oplus I$$

$$T_B = Q_A \cdot \bar{I} + \bar{Q}_B \cdot \bar{I} = \bar{I} (Q_A + \bar{Q}_B)$$


$$Z = Q_A \cdot Q_B + \bar{Q}_A \cdot \bar{Q}_B \cdot \bar{I}$$

(b) Mealy machine, ^{output} Z depends on ^{input} I directly


(c)

Q_A	Q_B	I	\bar{T}_A	K_A	T_B	Q_A^+	Q_B^+	Z
0	0	0	0	0	1	0	1	1
0	0	1	1	0	0	1	0	0
0	1	0	1	1	0	1	1	0
0	1	1	0	1	0	0	1	0
1	0	0	0	0	1	1	1	0
1	0	1	1	0	0	1	0	0
1	1	0	1	1	1	0	0	1
1	1	1	0	1	0	0	1	1

(d)

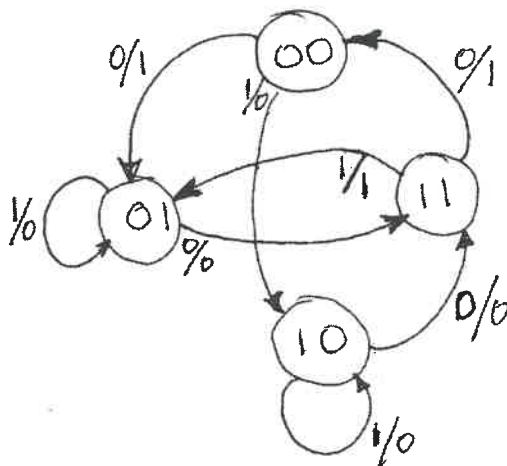


(e)

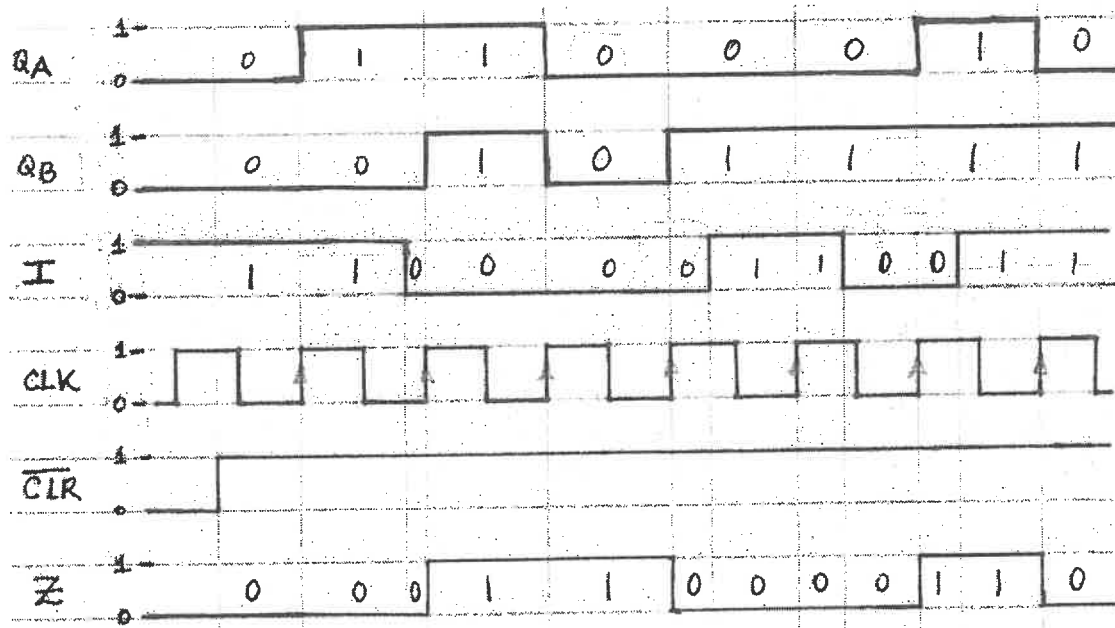

(a)

3

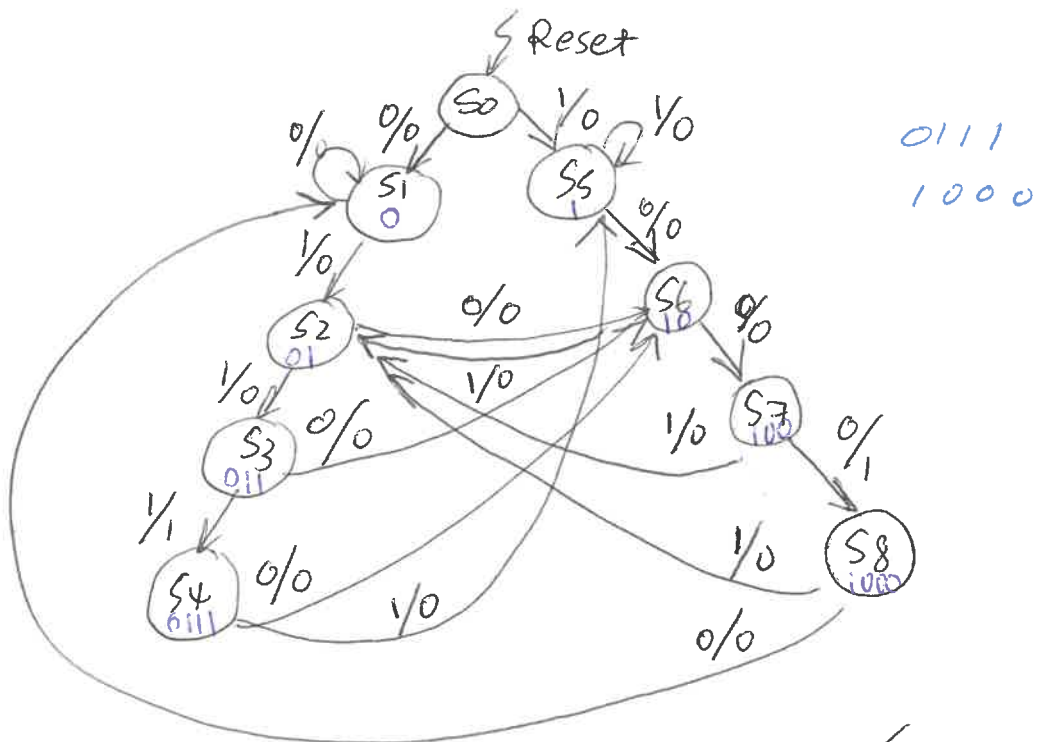

(b)


Present State	Next State / output Y	
	x=0	x=1
S0	S1 / 0	S5 / 0 S4 / 0
S1	S1 / 0	S2 / 0
S2	S6 / 0	S3 / 0
S3	S6 / 0	S4 / 1
S4	S6 / 0	S5 / 0 S4 / 0
S5	S6 / 0	S5 / 0
S6	S7 / 0	S2 / 0
S7	S8 / 1 S1 / 1	S2 / 0
S8	S1 / 0	S2 / 0

3

S1	S2-S5								
S2	S1-S6 S3-S5	S1-S6 S2-S3							
S3	X	X	X						
S4	S1-S6	S1-S6 S2-S5	S3-S5	X					
S5	S1-S6	S1-S6 S2-S5	S3-S5	X	✓				
S6	S1-S7 S2-S5	S1-S7 S1-S7	S6-S7 S2-S3	X	S2-S5 S6-S7	S6-S7 S2-S5			
S7	X	X	X	X	X	X	X		
S8	S2-S5	✓	S1-S6 S2-S3	X	S1-S6 S2-S5	S1-S6 S2-S5	S1-S7	X	1
	S0	S1	S2	S3	S4	S5	S6	S7	

$S1 \equiv S8$

$S4 \equiv S5$

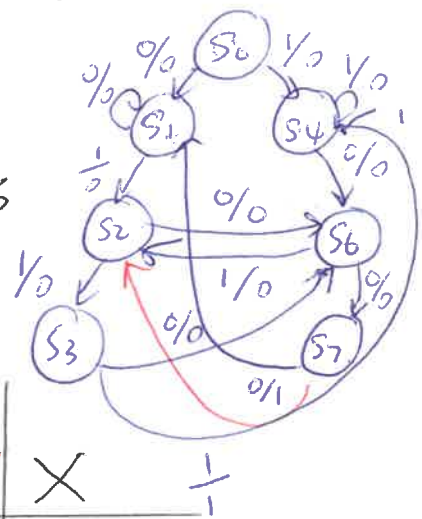

(C) Guideline #1: for $x=0$, $\{S_0, S_1, S_7\}$, $\{S_2, S_3, S_4\}$
 (States with same next state) for $x=1$, $\{S_0, S_3, S_4\}$, $\{S_1, S_6, S_7\}$

Guideline #2:
 (Next states of the same state)

$\{S_1, S_4\}$, $\{S_1, S_2\}$, $\{S_6, S_3\}$, $\{S_6, S_4\}$
 $\{S_7, S_2\}$, $\{S_1, S_2\}$

3


One possible assignment

c \ AB	00	01	11	10
0	S ₀	S ₇	S ₂	S ₃
1	S ₁	S ₆		S ₄

A B C	
S ₀ :	000
S ₁ :	001
S ₂ :	110
S ₃ :	100

A B C	
S ₄ :	101
S ₆ :	011
S ₇ :	010

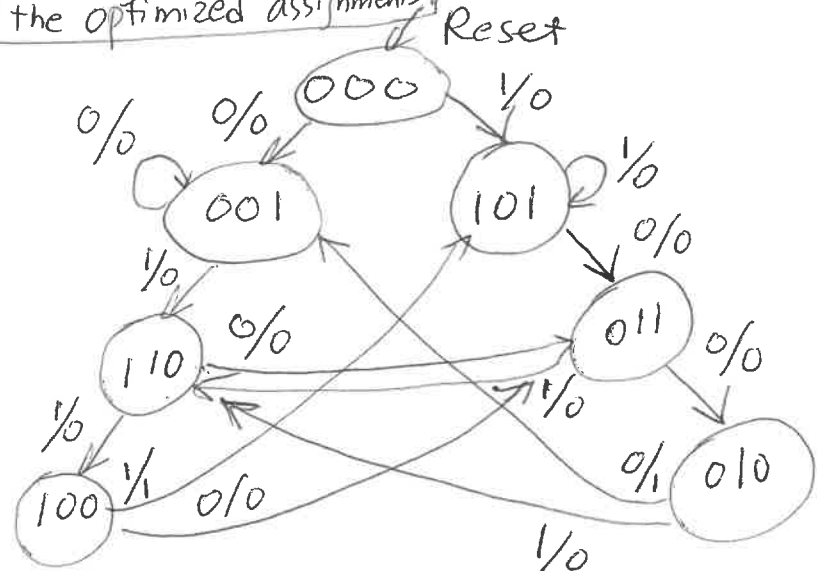Note: This assignment is just one of the optimized assignments.



(d)	A B C	A ⁺ B ⁺ C ⁺		Output Y	
		x=0	x=1	x=0	x=1
S ₀ :	0 0 0	001	101	0	0
S ₁ :	0 0 1	001	110	0	0
S ₂ :	1 1 0	011	100	0	0
S ₃ :	1 0 0	011	101	0	1
S ₄ :	1 0 1	011	101	0	0
S ₆ :	0 1 1	010	110	0	0
S ₇ :	0 1 0	001	110	1	0

CX \ AB	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	1	1	X	1
10	0	0	X	0

$A^+ = X$

CX \ AB	00	01	11	10
00	0	0	1	1
01	0	1	0	0
11	1	1	X	0
10	0	1	X	1

$B^+ = A\bar{X} + BC + \bar{A}BX + \bar{A}CX$

4

CX \ AB	00	01	11	10
00	1	1	1	1
01	1	0	0	1
11	0	0	X	1
10	1	0	X	1

$C^+ = \bar{C}\bar{X} + \bar{B}\bar{C} + A\bar{B} + \bar{B}\bar{X}$

CX \ AB	00	01	11	10
00	0	1	0	0
01	0	0	0	1
11	0	0	X	0
10	0	0	X	0

$Y = \bar{A}\bar{B}\bar{C}\bar{X} + A\bar{B}\bar{C}D$

(e)

1

