
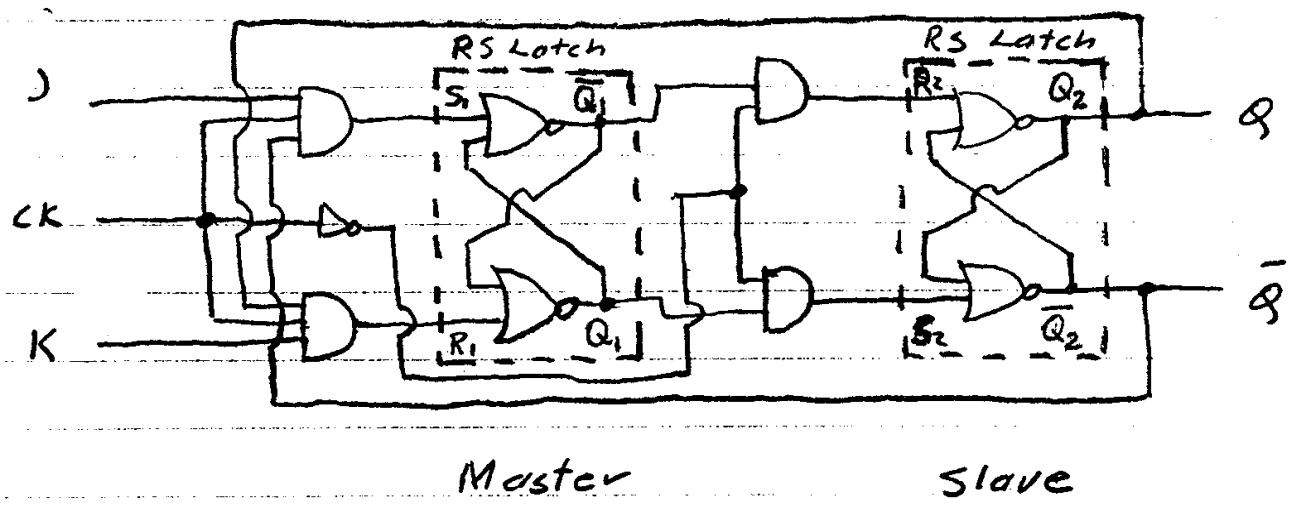


 1. (a) Draw the state transition diagram of the master-slave JK flip-flop below.
 States are defined by outputs $Q\bar{Q}$. Transitions are determined by the values on input terminals JK . When do these transitions happen, on the rising or falling edge of Ck ?




- (b) Modify the circuit to allow asynchronous PRESET and CLEAR operations.
 Are these inputs active high or active low?

2. Complete the following timing diagram for the JK flip-flop described above in 1(a) (i.e., sketch Q_1 and Q). Both Q_1 and Q start at logic '0' as can be observed in the diagram.



 3. (a) Draw the block diagram (two RS latches in tandem) and symbol for a D flip-flop that is “falling-edge triggered”; that is, the value of D is transferred to the output Q when Ck goes LOW.
- (b) Reproduce the waveforms for Ck and D (shown below) and draw the resulting waveforms for Q_1 and $Q_2 = Q$. Assume Q starts at logic ‘1’.



4. A 3-bit synchronous counter must advance through the sequence 111, 110, 101, 100, 000, 001, 010, 011, 111 and then repeat. Design the counter using
 - (a) JK flip-flops, and
 - (c) T flip-flops.
 Are the counter implementations self-starting? Explain.

5. The following circuit contains two JK flip-flops.
 - (a) Write the logic expressions for J_A , K_A , J_B and K_B .
 - (b) Obtain the state transition table for the circuit.
 - (c) Sketch the state transition diagram for the circuit.

