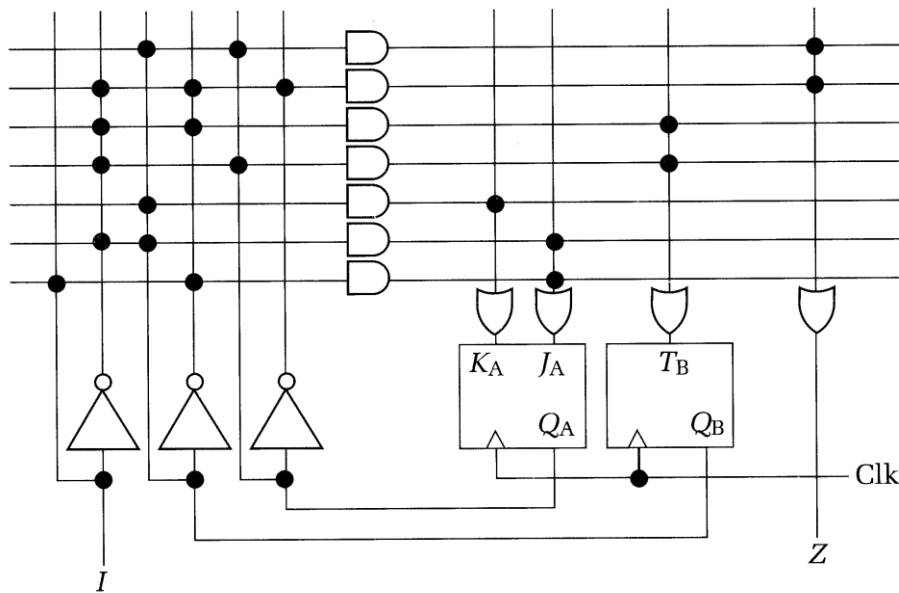


1. (a) Using the minimum 2-level SoP logic required, design a sequential circuit with three T flip-flops, A, B and C, and two inputs E and X that performs as follows:
  - If  $E = 0$  the circuit remains in the same state regardless the value of X,
  - When  $E = 1$  and  $X = 1$  the circuit goes through the state transitions 000 to 001 to 010 to 011 to 100 back to 000, and repeats,
  - When  $E = 1$  and  $X = 0$  the circuit goes through the state transitions 111 to 110 to 101 to 100 to 011 back to 111, and repeats.


- (b) Is the countup self-starting, *i.e.* if X remains at 1? Justify. Include state transition diagram.
- (c) Is the countdown self-starting, *i.e.* if X remains at 0? Justify. Include state transition diagram.

2. The finite state machine (FSM) shown in the figure below is implemented with one toggle (T) flip-flop and one JK flip-flop. It has one input I and one output Z. The combinational logic required for the next state and output functions is implemented by a PLA structure.

- (a) Write the logic expressions for  $J_A$ ,  $K_A$ ,  $T_B$  and Z.
- (b) Which of the two types of FSM seen in classes is this? Justify.
- (c) Obtain the state transition table including the output Z.
- (d) Draw the complete state transition diagram of the FSM.



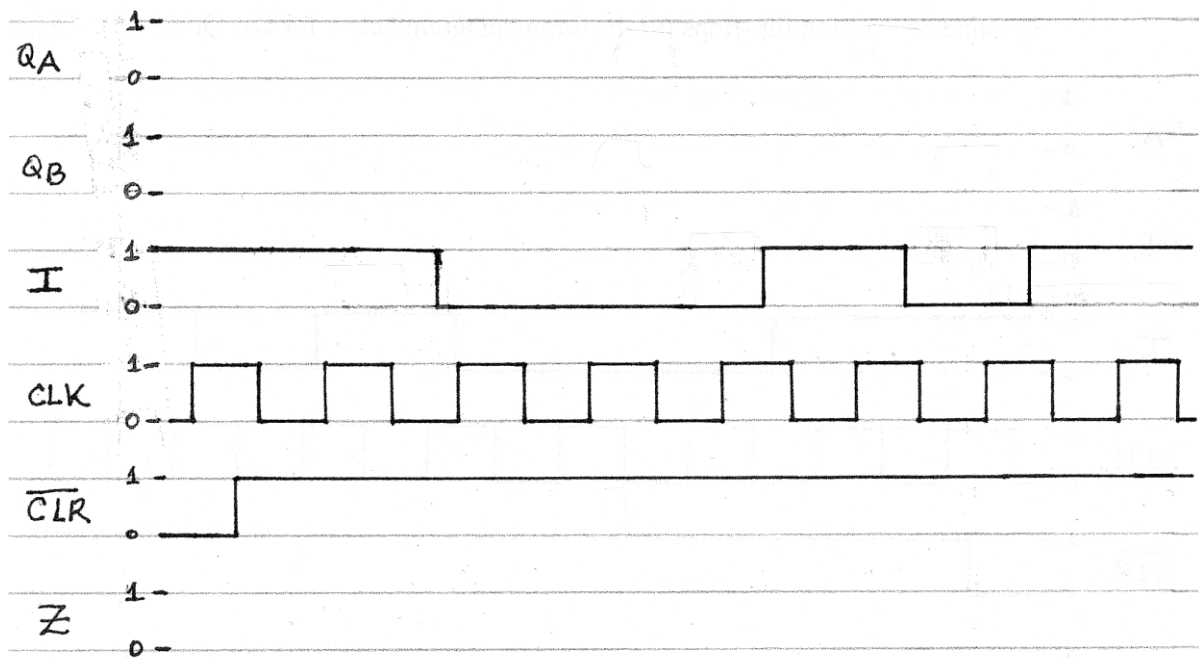- (e) Assuming the  $\overline{PR}$  is deasserted (HIGH) and the active-low clear  $\overline{CLR}$  below is connected to both flip-flops fill the timing diagram below for  $Q_A$ ,  $Q_B$  & Z.



3. Design a Mealy finite state machine controller for the simple vending machine example learnt in class (coursenotes pp. 217-226).