

Assignment #1 – ECED 4260


Note: Please include headers for the HDL code. Two example headers are provided below.

```

-----
-- Assignment 1. 4:1 Multiplexer                               /*
-- Author:    ECED 4260                                       A two-way light controller
-- Student ID: B00----- Author:    ECED 4260
-- Date:      September xx, 2024 Student ID:    B00-----
-- File Name: light.vhd   Date:    September xx, 2024
-- Architecture: Structural with 2:1 MUX File Name:    light.v
-- Description: ..... Description: The circuit can be used to....
-- Acknowledgements: Acknowledgements:
-----

```

 1. Build an HDL model of a 4-to-1 Multiplexer using 2-to-1 Multiplexer as components.
2. Design a Half Adder using VHDL or Verilog, and use it to build a Full Adder.



3. Design a Binary Coded Decimal (BCD) – to - 7-segment display decoder using VHDL or Verilog. The seven outputs of the decoder, *a* to *g*, are active high (i.e. a ‘1’ will light up the corresponding segment).



4. Build a finite state machine that detects the patterns of “1001” and “1101” from a serial bit stream, overlapping allowed. When the state machine detects the pattern, it will set its output signal to ‘1’ for a clock cycle.
 - (a) Draw the state transition diagram. Label all nodes and arcs.
 - (b) Derive the next state logic and the output logic equations.
 - (c) Write an HDL model of this FSM.
 - (d) Use ModelSim to simulate your pattern detector, and attach a screenshot of your simulation result.