

## Reference Solutions: Assignment #1 – ECED 4260

1. A 4-to-1 multiplexer using 2-to-1 multiplexer as components

VHDL examples:

```
library IEEE;
use IEEE.std_logic_1164.all;

entity Mux_4 is
    port (
        Input    : in std_logic_vector(3 downto 0);
        Sel      : in std_logic_vector(1 downto 0);
        Output   : out std_logic
    );
end Mux_4;

architecture structural of Mux_4 is
    component Mux_2
        port(
            Input    : in  std_logic_vector(1 downto 0);
            Sel      : in  std_logic;
            Output   : out std_logic
        );
    end component;
    -- Declare the signals needed in the entity
    signal internalMuxOut : std_logic_vector(1 downto 0);
begin
    -- Create three Mux_2 components and connect them accordingly
    Mux1: Mux_2 port map (Input(3 downto 2), sel(0), internalMuxOut(1));
    Mux2: Mux_2 port map (Input(1 downto 0), sel(0), internalMuxOut(0));
    Mux3: Mux_2 port map (internalMuxOut(1 downto 0), sel(1), Output);
end structural;
```

```
library IEEE;
use IEEE.std_logic_1164.all;

entity Mux_2 is
    port (
        Input    : in std_logic_vector(1 downto 0);
        Sel      : in std_logic;
        Output   : out std_logic
    );
end Mux_2;

architecture rtl of Mux_2 is
    -- Declare the signals needed in the entity.
    signal sel_bar : std_logic;
    signal andSel  : std_logic_vector(1 downto 0);
begin
    sel_bar    <= not Sel;
    andSel(0) <= sel_bar and Input(0);
    andSel(1) <= Sel and Input(1);
    Output    <= andSel(1) or andSel(0);
end rtl;
```

## Verilog MUX:

```
`timescale 1ns / 1ps

module Mux_4 (
    input [3:0] in,
    input [1:0] sel,
    output out);

    // Declare wires needed for entity
    wire [1:0] internalMuxOut;

    // Create the 3 mux components needed
    Mux_2 m1 (in[3:2], sel[0], internalMuxOut[1]);
    Mux_2 m2 (in[1:0], sel[0], internalMuxOut[0]);
    Mux_2 m3 (internalMuxOut[1:0], sel[1], out);
endmodule
```

endmodule

```
`timescale 1ns / 1ps



module Mux_2 (
    input [1:0] in,
    input sel,
    output out);

    wire sel_bar;
    wire [1:0] andsel;

    assign sel_bar = ~sel;
    assign andsel[0] = sel_bar & in[0];
    assign andsel[1] = sel & in[1];
    assign out = andsel[1] | andsel[0];
endmodule
```

endmodule

## 2. Half Adder and Full Adder:

  

```

/* Verilog halfadder */
module halfadder (
  input a,b,
  output Sum, Cout);
  assign Sum = a ^ b;
  assign Cout = a & b;
endmodule

/* Verilog fulladder */
module fulladder (
  input a,b,cin,
  output Sum, Cout);
  wire c1, c2, s1;

  halfadder HA1 (a, b, s1, c1);
  halfadder HA2 (s1, cin, Sum, c2);
  assign Cout = c1 | c2;
endmodule

```

```

----- VHDL Q3 Full Adder -----
library ieee;
use ieee.std_logic_1164.all;

entity fulladder is
  port (a,b, cin: in std_logic;
        sum, cout : out std_logic);
end fulladder;

architecture structural of fulladder is
  component halfadder
    port (a,b: in std_logic;
          sum, carry : out std_logic);
  end component;
  signal c1, c2, s1: std_logic;

  begin
  HA1 : halfadder port map (a, b, s1, c1);
  HA2 : halfadder port map (s1, cin, sum, c2);
  cout <= c1 or c2;
end structural;


----- VHDL Half Adder -----
library ieee;
use ieee.std_logic_1164.all;

entity halfadder is
  port (a,b: in std_logic;
        sum, carry : out std_logic);
end halfadder;

architecture dtfl of halfadder is
begin
  sum <= a xor b;
  carry <= a and b;
end dtfl;

```

 3. Design a Binary Coded Decimal (BCD) – to - 7-segment display decoder using VHDL or Verilog. The seven outputs of the decoder, *a* to *g*, are active high (i.e. a ‘1’ will light up the corresponding segment)



```

library ieee;
use ieee.std_logic_1164.all;

entity BCD_7Seg is
port (BCD: in std_logic_vector (3 downto 0);
      a, b, c, d, e, f, g: out std_logic);
end BCD_7Seg;

architecture behavioral of BCD_7Seg is
signal Seg: std_logic_vector (6 downto 0);
begin
with BCD select
  Seg <= "01111111" when "0000",
         "00001110" when "0001",
         "10110111" when "0010",
         "10011111" when "0011",
         "11001110" when "0100",
         "11011011" when "0101",
         "11111011" when "0110",
         "00001111" when "0111",
         "11111111" when "1000",
         "11011111" when "1001",
         "00000000" when others;

  a <= Seg (0);
  b <= Seg (1);
  c <= Seg (2);
  d <= Seg (3);
  e <= Seg (4);
  f <= Seg (5);
  g <= Seg (6);
end behavioral;

```

```

module BCD2 (BCD, a, b, c, d, e, f, g);
input [3:0] BCD;
output a, b, c, d, e, f, g;
reg [6:0] Seg;

always @ (BCD)
begin
  case (BCD)
    4'd0 : Seg = 7'b01111111;
    4'd1 : Seg = 7'b00001110;
    4'd2 : Seg = 7'b10110111;
    4'd3 : Seg = 7'b10011111;
    4'd4 : Seg = 7'b11001110;
    4'd5 : Seg = 7'b11011011;
    4'd6 : Seg = 7'b11111011;
    4'd7 : Seg = 7'b00001111;
    4'd8 : Seg = 7'b11111111;
    4'd9 : Seg = 7'b11011111;
    default : Seg = 7'b00000000;
  endcase
end


assign a = Seg [0];
assign b = Seg [1];
assign c = Seg [2];
assign d = Seg [3];
assign e = Seg [4];
assign f = Seg [5];
assign g = Seg [6];

endmodule


```

4 (a). Reference state diagrams:

Example 1. Moore FSM

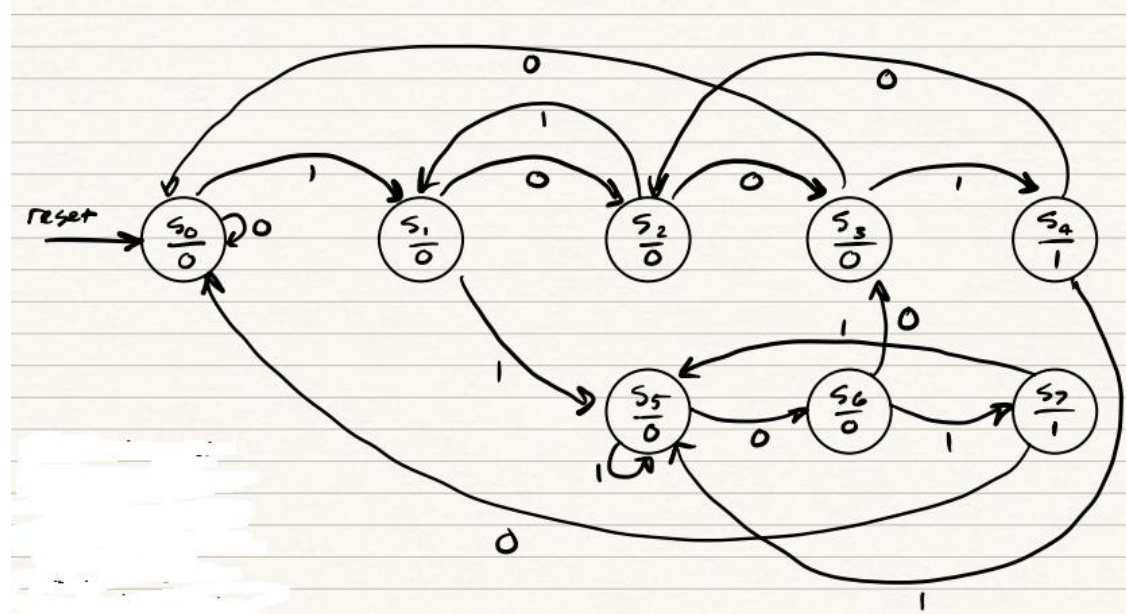

Example 2. Mealy FSM

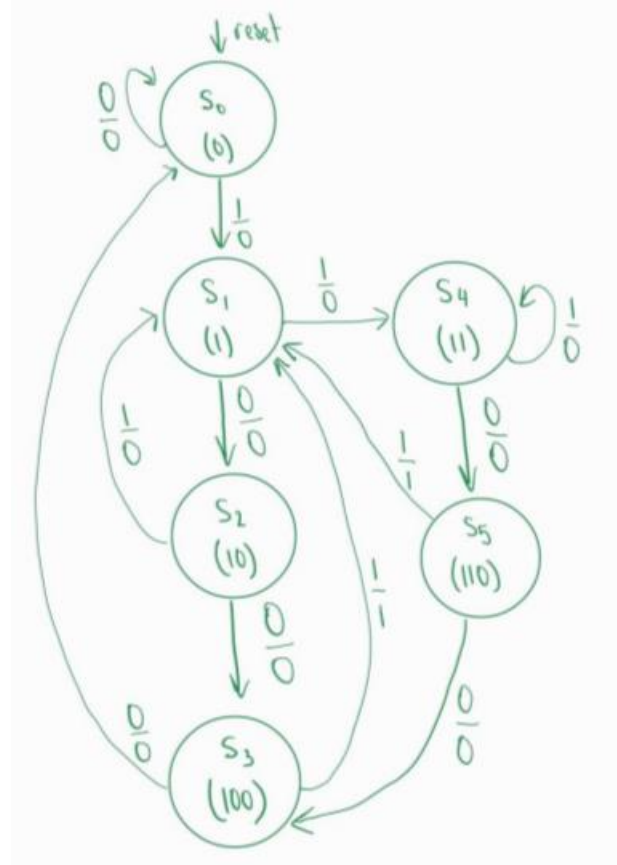

- 4 (b) (omitted) State optimization, binary state assignment, next-state and output logics.  
 4 (c)(d) Example Verilog Mealy FSM:

```

// overlapping pattern detector module
module overlappingPatternDetector(
  input wire clk, // input clock signal
  input wire rst, // input reset signal
  input wire in, // input bit
  output reg out, // output match flag
);
  // State encoding
  parameter S0 = 3'b000, S1 = 3'b001, S2 = 3'b010,
            S3 = 3'b011, S4 = 3'b100, S5 = 3'b101;

  // internal variables to store states
  reg [2:0] state, next_state;

  // State transition logic
  always @(posedge clk or posedge rst) begin
    if (rst)
      state <= S0; // Reset state
    else
      state <= next_state; // Move to next state
  end

  // Next state logic
  always @(*) begin
    case (state)
      S0: next_state = (in) ? S1 : S0; // S0 -> S1 if input = 1, else
stay in S0
      S1: next_state = (in) ? S4 : S2; // S1 -> S4 if input = 1, else
S2
      S2: next_state = (in) ? S1 : S3; // S2 -> S1 if input = 1, else
S3
      S3: next_state = (in) ? S1 : S0; // S3 -> S1 if input = 1, else
S0
      S4: next_state = (in) ? S4 : S5; // S4 -> S5 if input = 0, else
stay in S4
      S5: next_state = (in) ? S1 : S3; // S5 -> S1 if input = 1, else
S3
      default: next_state = S0; // Default state is S0
    endcase
  end

  // Output logic
  always @(posedge clk or posedge rst) begin
    if (rst)
      out <= 0; // reset output
    else
      out <= (state == S3 && in) || (state == S5 && in); // Output
logic
  end
endmodule

```

**Please note:**

You can code your FSM based on the optimized design from 4 (b):  
For example:

```
module '...' (clk,rst,I,O);
  input  clk,rst,I;
  output O;
  reg O;
  reg [2:0] state;

  parameter s0 = 3'b000,
            s1 = 3'b001,
            s2 = 3'b010,
            s3 = 3'b101,
            s4 = 3'b100;

  always@(posedge clk or posedge rst)
  begin
    if(rst == 1'b1)
    begin
      state <= s0;
      O <= 1'b0;
    end
    else
    begin
      case(state)
      s0:
        begin
```

.....

Sample waveform:

