

Department of Electrical & Computer Engineering
Dalhousie University

ECED 4260
IC Design and Fabrication
Midterm Examination

Instructor: Y. Ma
Exam date: Oct. 22, 2015
Exam duration: 80 minutes
Aids permitted: This is a closed book exam. No books or notes are to be consulted.
Two double-sided 8.5"x11" formula sheets are allowed.

- Instructions:
1. Provide your name printed, signature and I.D. number on this page.
 2. Verify that this booklet contains 8 pages (including the cover page).
 3. Neatly enter your answers in the spaces provided.
 4. Use the reverse sides of the pages for rough work.

Student name: _____

Signature: _____

Student ID: _____

Question	Time (min)	Worth	Mark	Subject
1	20	25		Combinational logic design
2	20	25		VHDL
3	20	25		Logic Simulation
4	20	25		Finite State Machine
Total	80 min	100		

Question 1. (25 marks)


Use JK flip-flops to design a finite state machine (FSM) that works as a 2-bit binary synchronous up-counter when its input $X=0$ and as a 2-bit binary synchronous down-counter when its input $X=1$.

- (a) (5 marks) Draw the state transition diagram.
- (b) (5 marks) Derive the next state equations.
- (c) (10 marks) Find minimized logic for the inputs of JK flip-flops.
- (d) (5 marks) Draw the resulting circuit that implements this FSM.

Question 1 (cont'd)

 Question 2. (25 marks)

Write a VHDL architecture for the entity below which implements a custom BCD to 7-segment decoder with the same output as assignment #1, also shown below. A darkened segment represents a '0'. Segment numbers are shown on the right.



7-segment display	0	1	2	3	4	5	6	7	8	9
Inputs: BCD	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001

```


ENTITY BCD_to_7segment IS
    PORT ( BCD: in bit_vector (3 downto 0);
          LED_display: out bit_vector (6 downto 0));
END BCD_to_7segment;

```

Question 2 (cont'd)

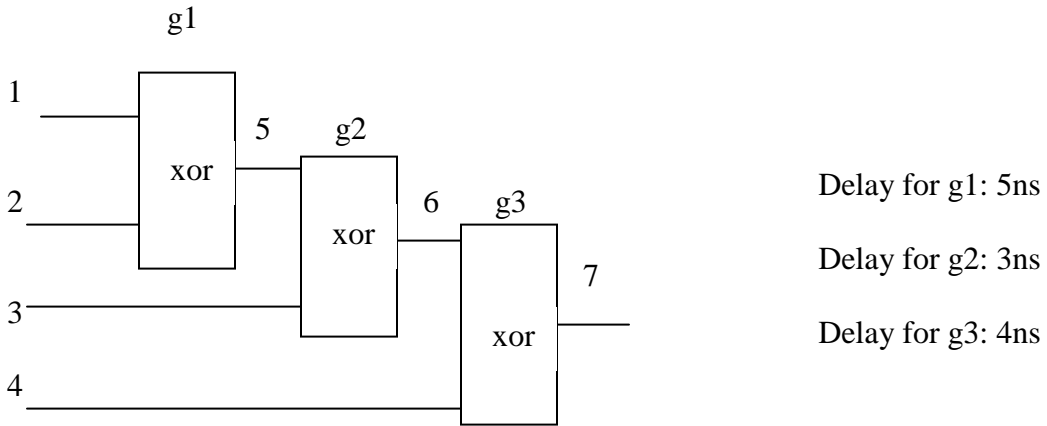Question 3. (25 marks)

The circuit given below is part of a larger system operating at a frequency of 200MHz. It was initialized by input $x_1x_2x_3x_4=0000$ at $t=0$, and all the circuit nodes are in known stable states. Perform the event-driven simulation of the circuit for two input vectors $x_1x_2x_3x_4=0101$ at the end of 1st clock cycle and $x_1x_2x_3x_4=0000$ at the end of second clock cycle. Complete the simulation table given below for $t=0$ to $t=20$, and derive the timing diagram from your simulation table. **Assume transport delay for all gates.**



(a) (18 marks) Complete the simulation table below

Time	Line values							Gates affected			Scheduled events
	1	2	3	4	5	6	7	g1	g2	g3	
init	0	0	0	0							

(b) (7 marks) Derive the wave-form timing diagram of all the circuits nodes.

1

2

3

4


5

6

7

 Question 4. (25 marks)

A finite state machine has one input x and one output z . The state transition diagram is shown below. The VHDL code given below describes part of the FSM architecture. By writing directly in the code, complete the architecture of this FSM with asynchronous reset.



```

library ieee;
use ieee.std_logic_1164.all;

entity example is
    port (clk, reset: in std_logic;
          x: in std_logic;
          z: out std_logic);

end entity example;

Architecture state_machine of example is
    Type stateType is (s0,s1,s2);
    Signal present_state, next_state: stateType;
Begin

Proc: process (present_state,x)

Begin
Case present_state is
    When s0 =>
        If (x='1') then Next_state <=s1; z <='0';
        Else Next_state <=s1; z <='1';
        End if;

        When s1 =>
        If (x='1') then Next_state <=s1; z<='0';
        Else Next_state <=s2; z<='0';
        End if;

        When s2 =>
        If (x='1') then Next_state <=s1; z <='1';
        Else Next_state <=s2; z <='0';
        End if;
End case;
End process Proc;

End architecture state_machine;

```