

Department of Electrical & Computer Engineering
Dalhousie University

ECED 4260
IC Design and Fabrication
Midterm Examination

Instructor: Y. Ma
Exam date: Oct. 26, 2006
Exam duration: 80 minutes
Aids permitted: This is a closed book exam. No books or notes are to be consulted.
Two double-sided 8.5"x11" formula sheets are allowed.

- Instructions:
1. Provide your name printed, signature and I.D. number on this page.
 2. Verify that this booklet contains 8 pages (including the cover page).
 3. Neatly enter your answers in the spaces provided.
 4. Use the reverse sides of the pages for rough work.

Student name: _____
Signature: _____
Student ID: _____

Reference Solution


Question	Time (min)	Worth	Mark	Subject
1	15	20		Boolean algebra
2	10	20		Combinational logic design
3	20	20		VHDL
4	20	20		Logic Simulation
5	15	20		Finite State Machine
Total	80 min	100		

Question 1. (20 marks)

1.1 (15 marks) Sometimes the XOR gates in a logic design need to be converted into their corresponding NAND implementation. For example, an ECED 4260 student and his/her lab partner may want to reduce the types of gates used in their design in order to reduce the number of chips in their lab circuit implementation. In practice, testing engineers may do the conversion to improve the testability of digital circuits. The Boolean expression given below describes the XOR function of variables a and b . Use Boolean algebra to manipulate the expression, so that f contains 2-input NAND logic only. No inversion or any other logic operations are allowed.

$$\begin{aligned} f &= a'b + ab' \\ &= \bar{a}b + a\bar{b} + a\bar{a} + b\bar{b} \\ &= a(\bar{a} + \bar{b}) + b(\bar{a} + \bar{b}) \\ &= \overline{a \cdot \bar{a}b + b \cdot \bar{a}b} \\ &= \overline{a \cdot \bar{a}b} \cdot \overline{b \cdot \bar{a}b} \end{aligned}$$


1.2 (5 marks) Draw the schematic diagram corresponding to your new f function.

 

Question 2. (20 marks)


2. Multiplexers are important constructs for RTL circuits. If you only have a 4-input 1-bit multiplexer available, can you implement the function, F , defined by the truth table given below? Draw the Mux and indicate the inputs.

		Q1Q2			
		00	01	11	10
Q3	0	0	1	1	0
	1	1	0	0	1

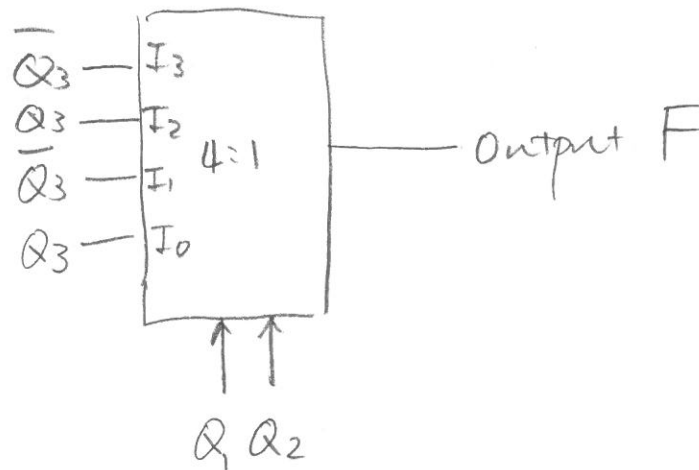

Question 3. (20 marks)

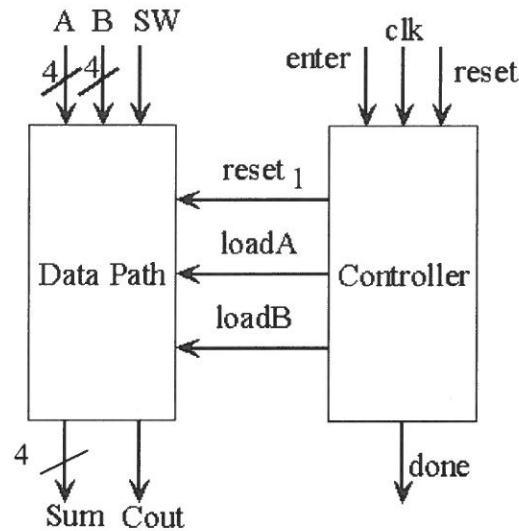3. The figure below shows the final design of the system. Assume that the architecture of data path and controller are available; write out the entities of Data Path and Controller and your final design entity and architecture.



```

library ieee;
use ieee.std_logic_1164.all;
  
```

```

entity final-design is
  port ( A, B: in std_logic_vector(3 downto 0);
        SW, enter, clk, reset: in std_logic;
        sum: out std_logic_vector(3 downto 0);
        cout, done: out std_logic);
end final-design;
  
```

Architecture structural of final-design is

```

component Data_Path
  port ( A, B: in std_logic_vector(3 downto 0);
        SW, reset1, loadA, loadB: in std_logic;
        sum: out std_logic_vector(3 downto 0);
        cout: out std_logic);
end component;
  
```

Question 3 (cont'd)

```
component Controller  
    port (enter, clk, reset: in std_logic;  
          reset1, loadA, loadB, done: out std_logic);  
end component;
```

```
signal reset1, loadA, loadB: std_logic;
```


Begin

```
myDatapath: component Data-Path  
    port map (A, B, SW, reset1, loadA, loadB, sum, cout);
```

```
myController: component Controller  
    port map (enter, clk, reset, reset1, loadA, loadB, done);
```


```
End structural;
```


4.2 Derive the wave-form timing diagram of all the circuits nodes. (5 marks)

 

Question 5. (20 marks)

 5.1 A finite state machine has one input x and one output z . The state transition diagram is shown below. Explain what the machine is supposed to do. (6 marks)



Pls. see Sample midterm 3: Q3

5.2 The VHDL code given below describes the above FSM with an extra output showing the binary assignment of the states.

(a) (7 marks) By writing directly in the code, show how to add Mealey output z to the state machine. Label these changes with (a).

(b) (7 marks) By writing directly in the code, indicate how an asynchronous reset can be added that causes transitions to the state s0. Label these changes with (b).

```
library ieee;
use ieee.std_logic_1164.all;

entity example is
    port (clk: in std_logic;
          x: in std_logic;
          stateout: out std_logic_vector (1 downto 0));
end entity example;

architecture state_machine of example is
    type statetype is (s0, s1, s2, s3);
    signal present_state, next_state: statetype;
begin
    comb_logic: process (present_state, x) begin
        Case present_state is
            when s0 => stateout<="00";
                If (x='1') then next_state<=s1;
                else next_state<=s0;
                end if;
            when s1 => stateout<="01";
                If (x='0') then next_state<=s2;
                else next_state<=s1;
                end if;
            when s2 => stateout<="10";
                If (x='1') then next_state<=s3;
                else next_state<=s0;
                end if;
            when s3 => stateout<="11";
                If (x='1') then next_state<=s1;
                else next_state<=s2;
                end if;
        end case;
    end process comb_logic;

    memory_element: process (clk) begin
        If (clk'event and clk='1') then
            present_state <= next_state;
        end if;
    end process memory_element;
end architecture state_machine;
```