

V. Digital System Testing

5. Digital System Testing

5.1 Introduction to Digital System Testing

5.2 Fault and Fault Models

5.3 Boundary Scan

5.1 Introduction to Digital System Testing

- Highlight of IC
 - LSI (1000), VLSI (100000) ULSI (1M)
 - Circuit densities: doubling every 18 month
 - Reliability up – better testing
 - Cost Down
 - Yield up
- Testing
 - Main purpose of fault testing is the detection of malfunctions
 - Location of the fault may also be desired

5.1 Introduction to Digital System Testing (cont'd)


- Why test IC
 - To verify design
 - To detect faults arising from manufacture or wear-out
 - To ensure components meet design specification (parameter)
- Cost of Testing
 - IC \$X
 - PCB board \$ 10X
 - System \$ 100X
 - Test cost $> 50\%$ production cost

5.1 Introduction to Digital System Testing (cont'd)

- Verification
 - A design is checked to meet the requirement and specifications
 - Functions test checks that the circuit implement the functions that is required, and does not implement the function that is not required
- Factors
 - Original design specifications
 - Delays, hazards
 - Routing, layout design rules
- Tools
 - Simulators : logic, timing, functions behavioral
 - HDL, VHDL

 5.1 Introduction to Digital System Testing (cont'd)

- Testability
 - Observability: the internal signals can be determined at the output
 - Controllability: producing an internal signal value by applying signals to inputs
- Testing method
 - Off-line: external + BIT(built in test)
 - On-line: BIT (built-in test)
 - Example
- Structural testing




5.1 Introduction to Digital System Testing (cont'd)

- Ideal Testing Environment
 - Store the truth table of the circuit
 - Apply all possible input combinations
 - Examine the output responses
- Real testing environment
 - Fault modeling
 - Model physical defects by a small number of faults
 - Test pattern generation
 - Generate a test pattern
 - Output response analysis
 - Analyze the circuit output without storing all the circuit responses
- Fault coverage
 - Number of detected faults/ number of faults modeled

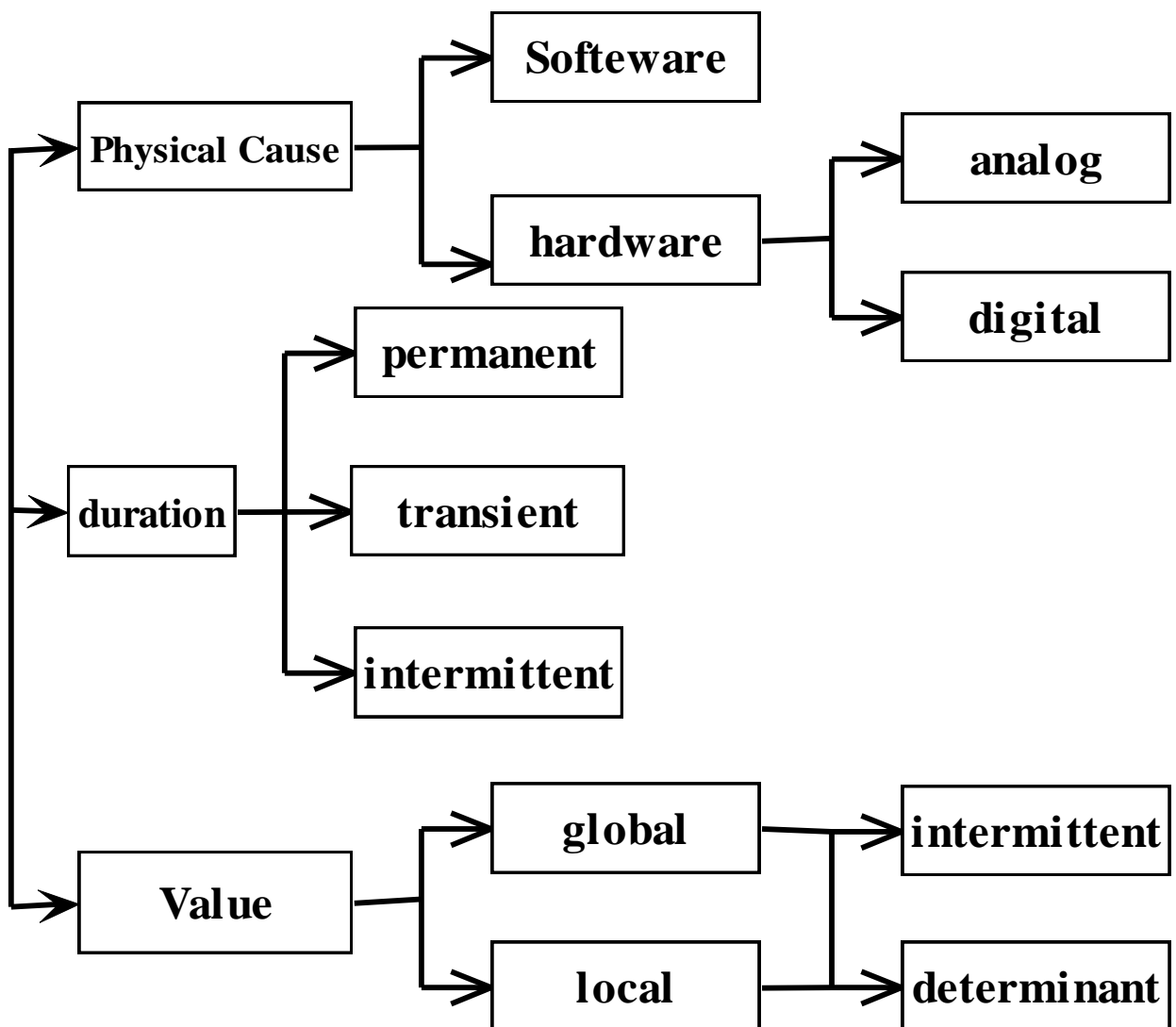5.2 Fault and Fault Models

- Before testing takes place, it is necessary to examine failure mechanisms, their effects and methods of modeling them




5.2 Fault and Fault Models

(cont'd)

- Fault characteristics:
 - Permanent fault– fault in existence long enough to be observed at test time
 - Transient fault: fault appears and disappears in short intervals of time
 - Intermittent fault: fault which appears and disappears at regular time intervals
- Faults models
 - A logical abstraction describing the functional effects of a physical failure
 - Different levels of modeling are used based on different primitives
 - Block: functional model, block diagram (data-path)
 - Gate: switching level, gates and latches
 - Circuit: electrical model, use transistors, resistors capacitors
 - Geometrical-model: layout description of chip ..

 
5.2.1 Stuck at Fault Model

- Most commonly used fault model
- May consider single or multiple stuck-at-faults
- The effect of the fault is modeled by having a line segment stuck at 0 or 1
 - All gates are perfect, problem may occur on line segments.
 - Single stuck at fault (SSF)
 - Example:
 - $\{x_1, x_2, x_3\}$: inputs $\{1, 2, 3, 4, 5, 6, 7, 8\}$: line segment number, F : correct output function, F^* incorrect output function



 5.2.1 Undetectable Faults


- Undetectable fault: its effect cannot be seen at the output, no matter what test pattern is applied




- Problem: redundancy may lead to undetectability
 - Why redundancy?
 - How to detect?
 - Undetectable faults may lead to problems in detecting other detectable faults

 5.2.1 Equivalent Faults

- What is equivalent faults?
- Example 1:




- Example 2:

 


 5.2.1 Equivalent Faults (cont'd)


- What is equivalent faults?
- Example 1:



- Example 2:

 


5.2.1 Equivalent Faults (cont'd)

 

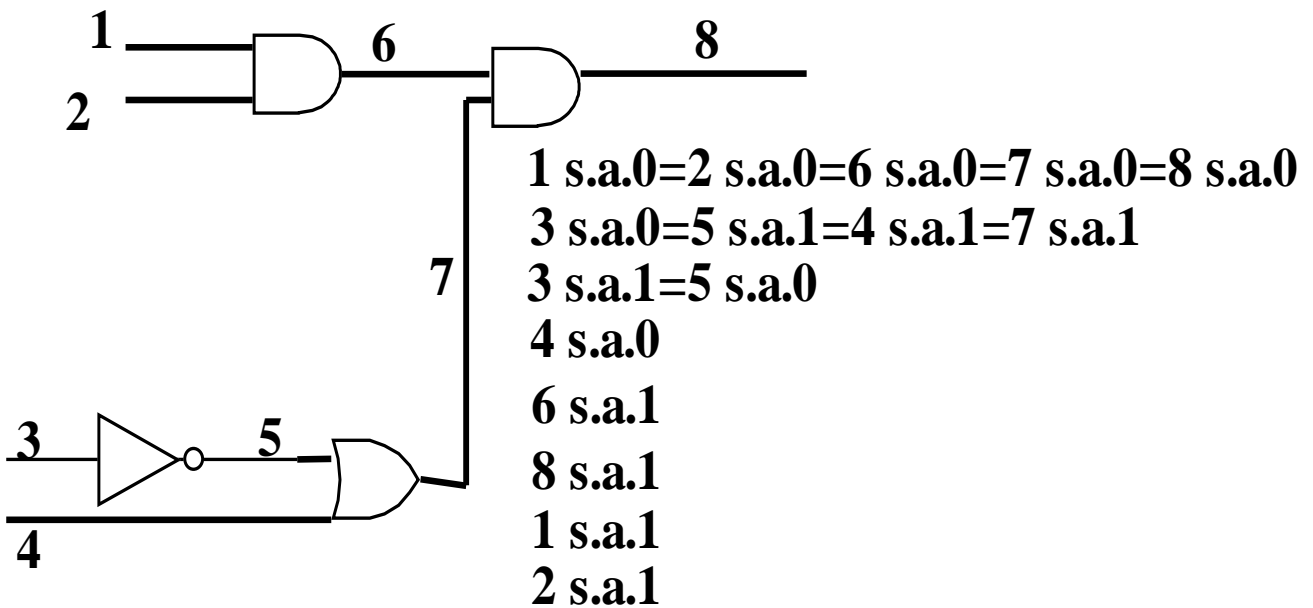5.2.2 Determine Test Pattern Generation

- Find a test vector for a given fault
 - Fault propagation
 - Path sensitization and backtracking




- 1/0 : 1234= 1101,1111,1100
- 3/0 : 1234= 1110
- 3/1 : 1234= 1100
- 4/0 : 1234 = 1111
- 6/1 : 1234 =
- For each of the test faults, find the test vectors
- Remove the redundant one, find the minimum set

 5.2.2 Determine Test Pattern Generation (cont'd)

Fault equivalence depends on individual gates

- AND any input/0 \leftrightarrow output/0
- Or any input/1 \leftrightarrow output/1
- NAND any input/0 \leftrightarrow output/1
- NOR any input/1 \leftrightarrow output/0
- NOT any input/0 \leftrightarrow output/1
- any input/1 \leftrightarrow output/0




5.2.2 Determine Test Pattern Generation (ATPG)

- Given a circuit of n line segments
 - There are $2n$ single stuck at faults
 - Fault collapsing reduces $2n$ faults to k faults
 - For each of the k faults, find a test vectors
 - Find a minimal test set from the test vectors that detect the k faults
- Advantages:
 - Short test length
 - 100% fault coverage
- Disadvantages:
 - very computational expensive
 - Need to store test vectors

 5.2.3 Pseudorandom Test Pattern Generation

- Using an autonomous linear feedback shift register (ALFSR)




$$P(X) = X^3 + X + 1$$

Time	S0	S1	S2
T1	0	0	1
T2	1	1	0
T3	0	1	1
T4	1	1	1
T5	1	0	1
T6	1	0	0
T7	0	1	0

5.2.3 Pseudorandom Test Pattern Generation (cont'd)


- Given a degree n $P(X)$ in binary field
 - Degree $n \rightarrow n$ stage ALFSR
 - If an ALFSR cycles through all $2^n - 1$ non zero states, it has the maximum length cycle, the corresponding $P(x)$ is primitive. Otherwise, it is non primitive
 - Example :
 - $P(x) = X^7 + X^3 + X^2 + 1$
 - Pseudorandom Test Pattern Generation (PTPG)
 - Advantages: easy to generate
 - No need for storage
 - Suitable for built-in self test
 - Disadvantages:
 - Relative long test length
 - Some faults may not be tested?
- Solution
 - DO PTPG cover 90-95%
 - DO ATPG cover rest

 5.2.4 An Off-line Test (signature analysis)




5.2.4 An Off-line Test (Cont'd)

- Example

 


$$F = AB + \bar{B}C$$

5.2.4 An Off-line Test (Cont'd) example

 

Time	S ₀	S ₁	S ₂	f
T1	0	0	1	1
T2	1	1	0	1
T3	0	1	1	0
T4	1	1	1	1
T5	1	0	1	1
T6	1	0	0	0


5.2.4 An Off-line Test (Cont'd) example

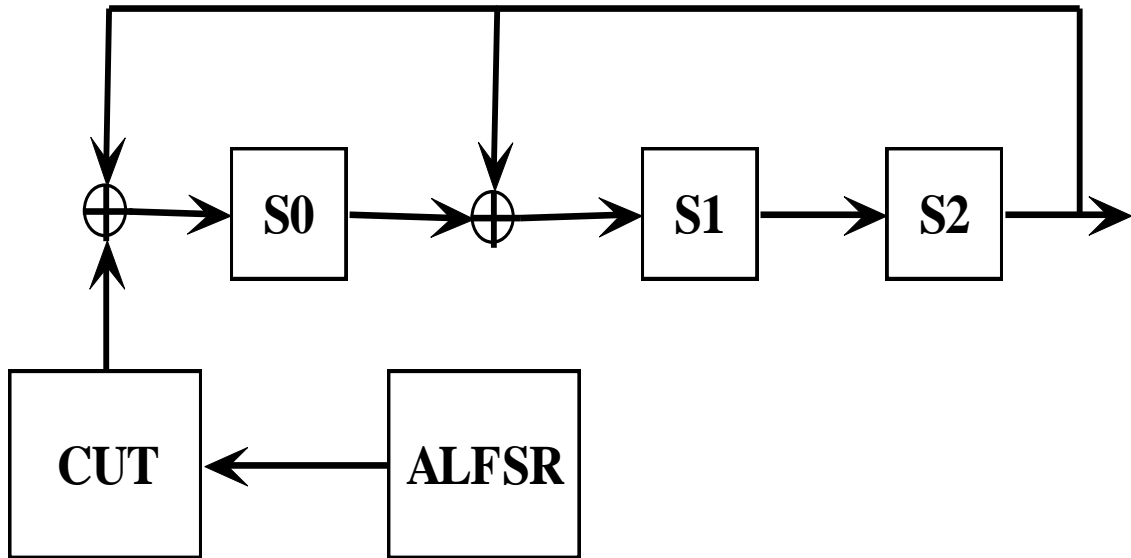

Time	f	S ₀	S ₁	S ₂
T ₀	--	0	0	0
T ₁	1	1	0	0
T ₂	1	1	1	0
T ₃	0	0	1	1
T ₄	1	0	1	1
T ₅	1	0	0	1
T ₆	0	1	1	1

- At T₆, s₀s₁s₂=111 is a fault free signature₂₇₃

5.2.4 An Off-line Test (Cont'd) example

 

5 s.a.1 $F^* = A + \bar{B}C$

Time	S ₀	S ₁	S ₂	f
T1	0	0	1	1
T2	1	1	0	1
T3	0	1	1	0
T4	1	1	1	1
T5	1	0	1	1
T6	1	0	0	1

5.2.4 An Off-line Test (Cont'd) example

- At T6, $s_0s_1s_2=011$ is a fault signature
- Fault is detected.

Time	f	S ₀	S ₁	S ₂
T0	--	0	0	0
T1	1	1	0	0
T2	1	1	1	0
T3	0	0	1	1
T4	1	0	1	1
T5	1	0	0	1
T6	1	0	1	1

5.3 Boundary Scan

- A design and test technique that allows circuits to be tested via the board edge connectors
 - I/O hardware is modified in design to incorporate a programmable shift register
 - Overhead minimal as it uses some empty space around I/O pads
- Problems of board test
 - Increasing IC complexity
 - Increasing use of surface-mount technology

5.3 Boundary Scan (cont'd)

- Inclusion of programmable shift register stage adjacent to each I/O pin such that signals at component boundaries can be controlled and observed using scan testing principles

